

Mid2-Grading Rubric


VE215 - Introduction to Circuits, Sung-Liang Chen Autumn 2019

1 Q1 (16pts)

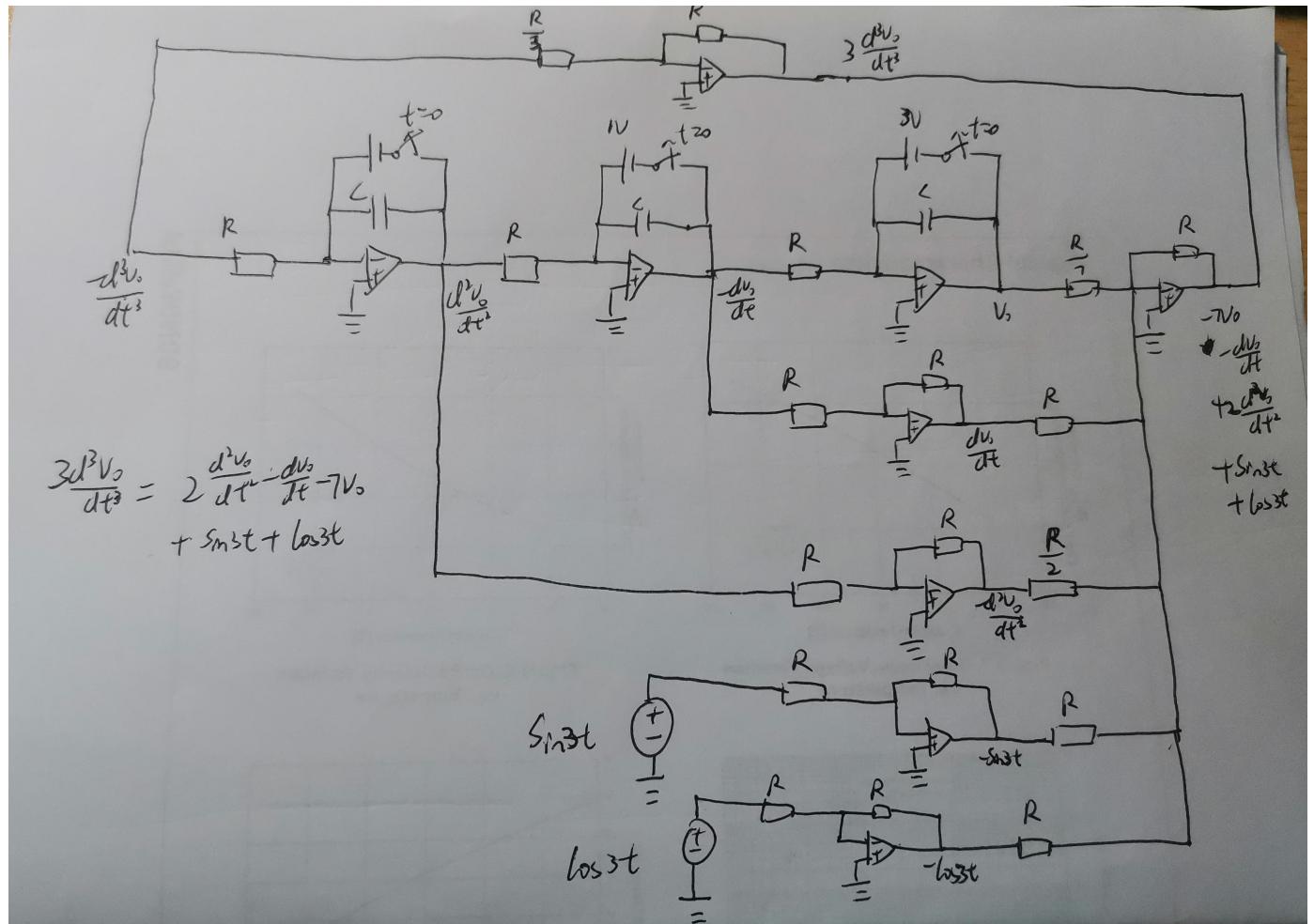1. Design an analog computer to simulate (16pts)


$$3\frac{d^3v_0}{dt^3} - 2\frac{d^2v_0}{dt^2} + \frac{dv_0}{dt} + 7v_0 = \sin 3t + \cos 3t$$

where $v_0''(0) = -1$, $v_0'(0) = 1$ and $v_0(0) = -3$



2 Q2 (16pts)

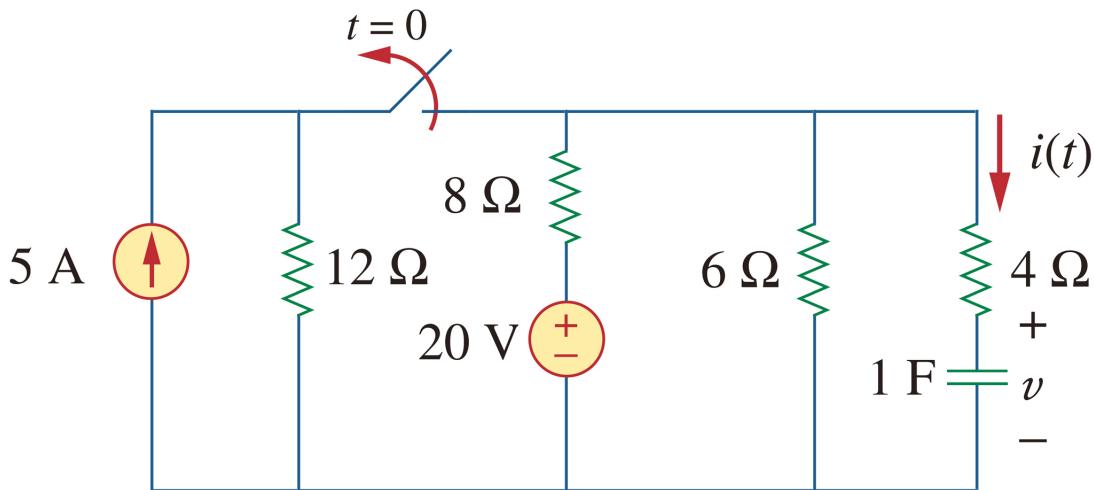2. For the circuit below, find $i(t)$ for $t > 0$. (16 pts)



$$v(0) : \frac{v}{12} + \frac{v-20}{8} + \frac{v}{6} = 5, v(0) = 20V$$

$$v(0^-) = v(0^+) = 20V \quad (4\text{pts})$$

$$v(\infty) : \frac{v}{6} + \frac{v-20}{8} = 0, v(\infty) = \frac{60}{7}V \approx 8.57V \quad (4\text{pts})$$

Find τ : (4pts)

I:

$$R_{eq} = 8//6 + 4 = \frac{24}{7} + 4 = \frac{52}{7}\Omega$$

$$\tau = RC = \frac{52}{7} \times 1 = \frac{52}{7}$$

II:

or by differential equation

$$\frac{v + \frac{dv}{dt} \times 4}{6} + \frac{v + \frac{dv}{dt} \times 4 - 20}{8} + \frac{dv}{dt} = 0$$

$$(\frac{1}{6} + \frac{1}{8})v + (\frac{2}{3} + \frac{1}{2} + 1)\frac{dv}{dt} = 2.5$$

$$\frac{7}{24}v + \frac{13}{6}\frac{dv}{dt} = 2.5$$

$$v(t) = 8.57 + (20 - 8.57)e^{-\frac{t}{\frac{52}{7}}}$$


$$= 8.57 + 11.43e^{-\frac{7}{52}t} \quad (2\text{pts})$$

$$i(t) = C \frac{dv}{dt} = -\frac{7}{52} \times 11.43 \times e^{\frac{7}{52}t}$$

$$= -1.54e^{-\frac{7}{52}t} \quad (2\text{pts})$$

3 Q3 (17pts)

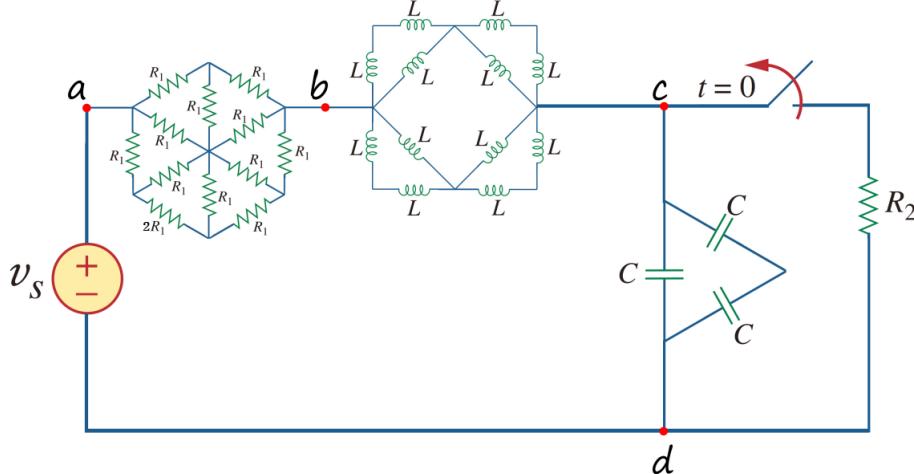- 3.(a) For the circuit below, find resistance from a to b, R_{ab} in terms of R_1 ; (4pts)
 (b) Find inductance from b to c L_{bc} in terms of L; (3pts)
 (c) Find capacitance from c to d C_{cd} in terms of C; (2pts)
 (d) When $V_s=11V$, $R_2=1\Omega$, $L=2H$, $C=0.5F$, for what values(or range) of R_1 will V_{cd} reach steady state most quickly?
 Find V_{cd} for $t > 0$ in this condition (select a value for R_1 if its in a range) and sketch V_{cd} for $t > 0$. (8pts)



3.1 a

$R_{ab} (a):$

$$R_{12} = \frac{3R_1}{2R_1 + 3R_1} = \frac{3R_1}{5R_1} = \frac{3}{5}R_1$$

$$R_{23} = \frac{3R_1}{2R_1 + 3R_1} = \frac{3R_1}{5R_1} = \frac{3}{5}R_1$$

$$R_{34} = \frac{3R_1}{2R_1 + 3R_1} = \frac{3R_1}{5R_1} = \frac{3}{5}R_1$$

$$\frac{R_1 + 2R_1 + 2R_1 + R_1 \cdot R_1}{2R_1 + 3R_1} = \frac{5R_1}{5R_1} = 1$$

$$\frac{R_1 + 2R_1 + 2R_1 + R_1 \cdot R_1}{R_1} = 5$$

$$R_{ab} = \frac{3R_1}{5R_1} = \frac{3}{5}R_1$$

$R_{ab} = 0.76R_1$

$R_{bc} (b):$

$$R_{bc} = \frac{\frac{15}{26}R_1}{\frac{15}{26}\frac{3}{5}R_1 + \frac{15}{26}\frac{15}{23}R_1 + \frac{15}{23}\frac{3}{5}R_1} = \frac{\frac{15}{26}R_1}{\frac{15}{26}R_1} = 1$$

$$R_{bc} = \frac{15}{26}R_1$$

$R_{cd} (c):$

$$R_{cd} = \frac{\frac{15}{26}\frac{3}{5}R_1 + \frac{15}{26}\frac{15}{23}R_1 + \frac{15}{23}\frac{3}{5}R_1}{\frac{15}{23}R_1} = \frac{\frac{15}{26}\frac{3}{5}R_1}{\frac{15}{23}R_1} = \frac{15}{26}\frac{3}{5}R_1 = \frac{11}{65}R_1$$

$$R_{cd} = \frac{11}{65}R_1$$

$R_{ab} = 0.76R_1$

$$R_{ab} \approx 0.76R_1$$

3.2 b

$$\begin{aligned} L//2L &= \frac{2}{3}L \\ \frac{2}{3}L + \frac{2}{3}L &= \frac{4}{3}L \\ L_{bc} = \frac{4}{3}L // \frac{4}{3}L &= \frac{2}{3}L. \quad (3\text{pts}) \end{aligned}$$

3.3 c

$$\begin{aligned} \frac{C \times C}{C+C} &= \frac{C}{2} \\ C_{cd} = \frac{C}{2} // C &= \frac{3}{2}C \quad (2\text{pts}) \end{aligned}$$

3.4 d

This is a series RLC circuit. $L_{bc} = \frac{2}{3}L = \frac{4}{3}H$, $C_{cd} = \frac{3}{2}C = \frac{3}{4}F$

$$\alpha = \frac{R}{2L}, \omega = \frac{1}{\sqrt{LC}}$$

As V_{cd} reaches steady state most quickly, it should be critically damped.

$$\text{Therefore, } \alpha^2 - \omega^2 = 0. \quad R = 2\sqrt{\frac{L_{bc}}{C_{cd}}} = 2\sqrt{\frac{\frac{4}{3}H}{\frac{3}{4}F}} = \frac{8}{3}\Omega$$

$$\text{Since } R = 0.76R_1, R_1 = \frac{200}{57}\Omega \approx 3.509\Omega \quad (2\text{pts})$$

$$\text{When } t < 0, V_{cd}(0^-) = \frac{11V}{\frac{8}{3}+1} \times 1 = 3V$$

$$V_{cd}(0^-) = V_{cd}(0^+) = 3V$$

$$i_{cd}(0) = \frac{11V}{1\Omega + \frac{8}{3}\Omega} = 3A$$

$$V_{ss} = V_{cd}(\infty) = 11V$$

$$\alpha = \frac{\frac{8}{3}\Omega}{2 \times \frac{4}{3}H} = 1$$

$$\text{Let } V_{cd} = V_{ss} + (A_1 + A_2t)e^{-\alpha t} = V_{ss} + (A_1 + A_2t)e^{-\alpha t} = 11V + (A_1 + A_2t)e^{-t}$$


$$i(0): C \frac{dv}{dt} = i(0) \text{ so that } C(-A_1e^{-t} + A_2e^{-t} - A_2te^{-t}) = 3 \text{ when } t=0. \text{ Then } -A_1 + A_2 = 4.$$

$$v(0) : 11 + A_1 = 3. \text{ Then } A_1 = -8$$

$$\text{Thus } A_2 = -4$$

$$\text{So } V_{cd} = [11 + (-8 - 4t)e^{-t}]V \quad (3\text{pts})$$

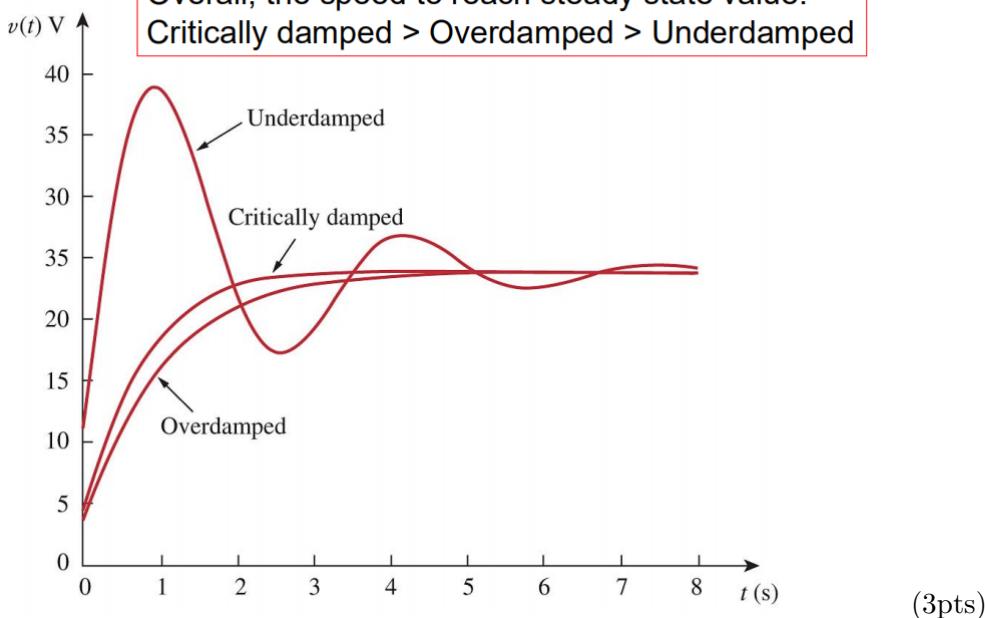Overall, the speed to reach steady state value:
Critically damped > Overdamped > Underdamped



4 Q4 (17pts)


(a) Write down three forms of Z, mark each form by its name. (3 pts)

For the circuit below,

(b) Determine the equivalent impedance of the circuit between a and b (6pts)

(c) The frequency of V_i is 50Hz. Determine V_0 when R is maximum, state whether the phase side is leading or lagging (4pts)

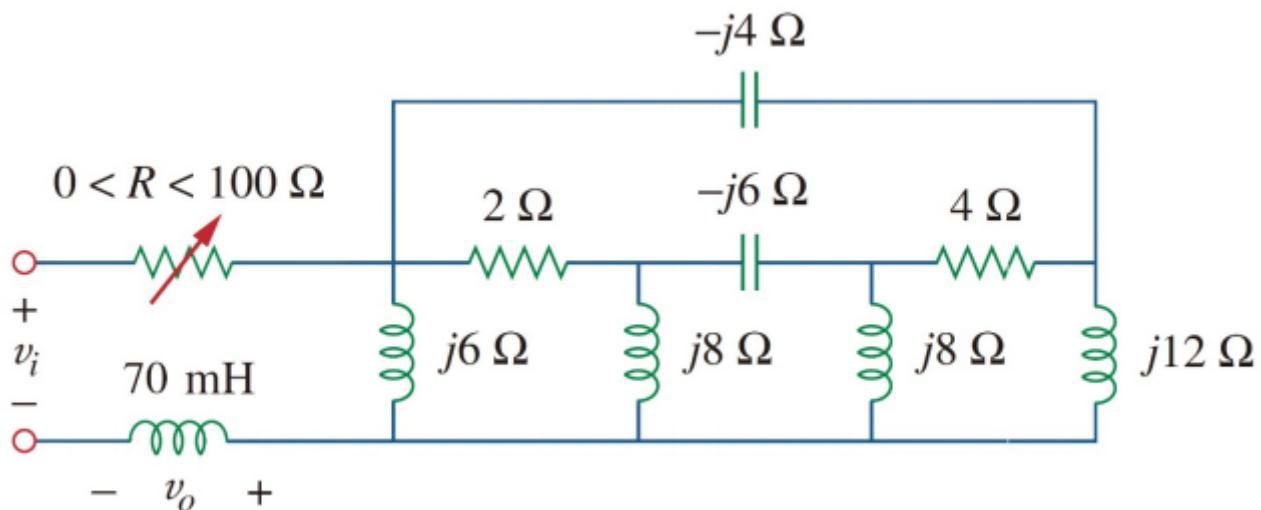(d) Find the value of R that will produce a phase shift of 75° of V_0 (4pts)



4.1 a

$$Z = x + jy \text{ rectangular form (1')}$$

$$Z = r\angle\phi \text{ polar form (1')}$$

$$Z = re^{j\phi} \text{ exponential form (1')}$$

4.2 b

Q4. b1.

$$\begin{aligned} & j6z // (3.574 + j6.69j) \\ &= 0.740 + j3.371b \\ & -j4z // (1.5 - j7.25) \\ &= 0.186 - j2.60j \\ & j12 // (11.727 + j8.94j) \\ &= 0.563 + j5.172j \\ & Z_{eq} = (0.740 + j3.371b) // \\ & [(0.186 - j2.60j) + (0.563 + j5.172j)] \\ &= (0.740 + j3.371b) // \\ & (0.744 + j2.572j) \\ &= 0.3790 + j1.46j \\ & \approx (0.38 + j1.46j) \Omega \end{aligned}$$

$$Z_{eq} = 0.38 + 1.46j \Omega$$

4.3 c

For 70mH , $j\omega L = j \times 2\pi(50\text{Hz}) \times 0.07\text{H} \approx j22\Omega$ (2')
When $R = 100\Omega$, $V_0 = V_i \angle 0^\circ \times \frac{j22}{100+0.38+j1.46+j22} = \frac{V_i \angle 0^\circ \times j22}{100.38+j23.46} = \frac{22V_i \angle 90^\circ}{103.08 \angle 13.14^\circ} = 0.213V_i \angle 76.86^\circ$ so that V_o leads V_i by 76.86° (2')

4.4 d

To produce a phase shift of 75° , the phase of $V_0 = 90^\circ + 0^\circ - \alpha = 75^\circ$

Hence $\alpha = \text{phase of } (R + 0.38 + j23.46) = 15^\circ$ (2')


For α to be 45° , $\frac{R+0.38}{23.46} = \tan 75^\circ$

Therefore, $R + 0.38\Omega = 87.5539\Omega$, $R = 87.1743\Omega \approx 87.17\Omega$ (2')

5 Q5 (17pts)

Refer to the oscillator below

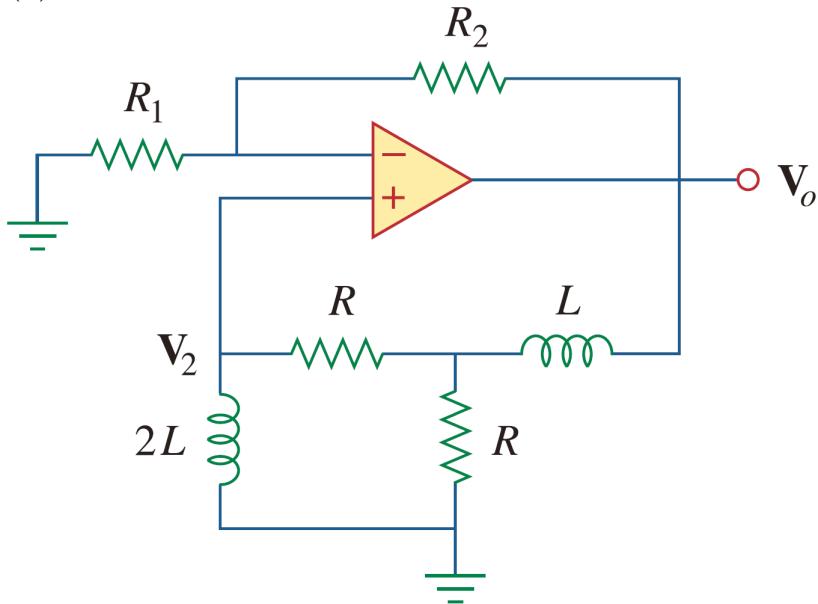- Determine $\frac{V_2}{V_0}$
- Determine the oscillation frequency f_0
- Obtain the relationship between R_1 and R_2 in order for oscillation to occur.



5.1 a

$$\frac{V_2}{2j\omega L} = \frac{V_1}{2j\omega L + R} \quad (1')$$

$$V_2 = \frac{2j\omega L}{2j\omega L + R} V_1 \quad (2')$$

$$\text{By applying KCL, } \frac{V_0 - V_1}{j\omega L} = \frac{V_1}{R + 2j\omega L} + \frac{V_1}{R} \quad (2'')$$

$$\frac{V_2}{V_0} = \frac{2}{4 + 2j\omega L/R + R/j\omega L}$$

$$\frac{V_2}{V_0} = \frac{2}{4 + j(2\omega L/R - R/\omega L)} \quad (2''')$$

5.2 b

$$\frac{2\omega_0 L}{R} - \frac{R}{\omega_0 L} = 0 \quad (2'')$$

$$\omega_0 = 2\pi f_0 = \frac{\sqrt{2}R}{2L} \quad (1'')$$

$$f_0 = \frac{\sqrt{2}R}{4\pi L} \quad (2'')$$

5.3 c


$$\text{When } \omega = \omega_0, \frac{V_2}{V_0} = \frac{1}{2} \quad (2'')$$

$$\text{Thus, } A_v = 1 + \frac{R_2}{R_1} = 2 \quad (1'')$$

$$\text{Therefore, } R_2 = R_1 \quad (2'')$$

6 Q6 (17pts)

6.1 Using Differential Equations

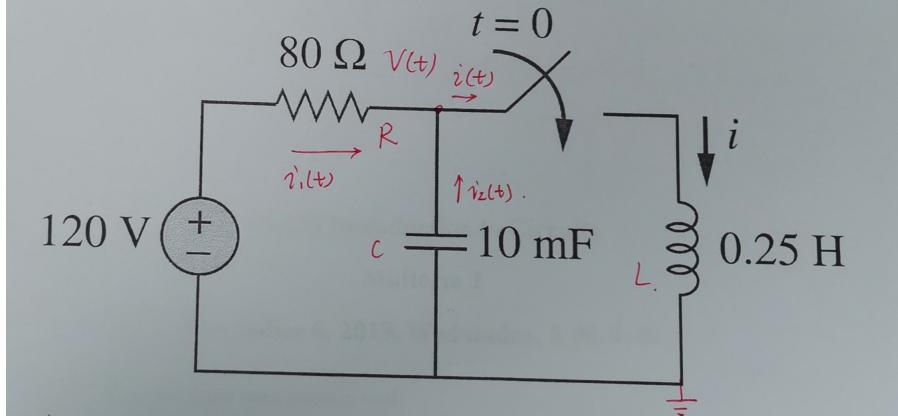

$$L \frac{di(t)}{dt} = v(t) \quad (3')$$

KVL: $i_1(t) = [120 - v(t)] \cdot \frac{1}{R} \quad (3')$

$$-C \frac{dv(t)}{dt} = i_2(t) \quad (3')$$

KCL: $i(t) = i_1(t) + i_2(t) = [120 - L \frac{di(t)}{dt}] \cdot \frac{1}{R} - C \cdot L \cdot \frac{d^2i(t)}{dt^2} \quad (3')$

$$i(t) = 1.5 - 3.125 \times 10^{-3} \cdot \frac{di(t)}{dt} - 2.5 \times 10^{-3} \cdot \frac{d^2i(t)}{dt^2} \quad (3')$$

$$i(t) \quad (1') = 1.5 \quad (1') - 3.125 \times 10^{-3} \frac{di(t)}{dt} \quad (1') - 2.5 \times 10^{-3} \cdot \frac{d^2i(t)}{dt^2} \quad (2')$$

or $i(t) = \frac{3}{2} - \frac{1}{320} \frac{di(t)}{dt} - \frac{1}{400} \cdot \frac{d^2i(t)}{dt^2}$

where $i_0(t) = 0, \frac{di_0(t)}{dt} = 480A/s$

6.2 Source Transformation + Formula for Parallel RLC Circuit

1.5A current source calculated (5')

Figure for source transformation (5')

$$\frac{d^2i}{dt^2} + \frac{1}{RC} \cdot \frac{di}{dt} + \frac{i}{LC} = \frac{1.5A}{LC}$$

$$\frac{d^2i}{dt^2} + \frac{4}{5} \frac{di}{dt} + 400i = 600 \quad (7')$$

$$i(t) = \frac{3}{2} - \frac{1}{320} \cdot \frac{di(t)}{dt} - \frac{1}{400} \cdot \frac{d^2i(t)}{dt^2}$$