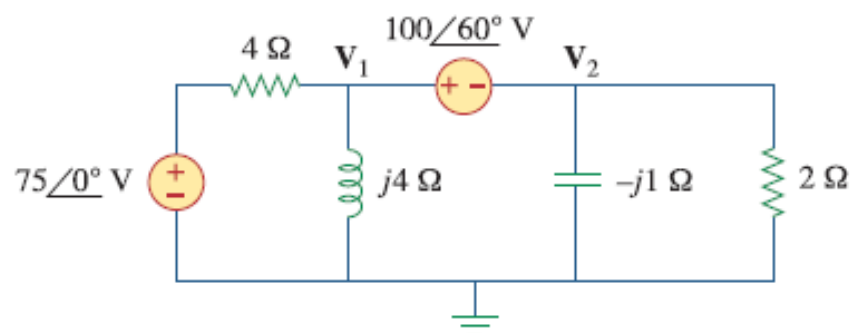


C10 problems

Calculate  $\mathbf{V}_1$  and  $\mathbf{V}_2$  in the circuit shown in Fig. 10.6.

## Practice Problem 10.2



**Figure 10.6**


For Practice Prob. 10.2.

**Answer:**  $\mathbf{V}_1 = 96.8 \angle 69.66^\circ \text{ V}$ ,  $\mathbf{V}_2 = 16.88 \angle 165.72^\circ \text{ V}$ .

Calculate current  $\mathbf{I}_o$  in the circuit of Fig. 10.11.

**Answer:**  $6.089 \angle 5.94^\circ \text{ A}$ .

## Practice Problem 10.4

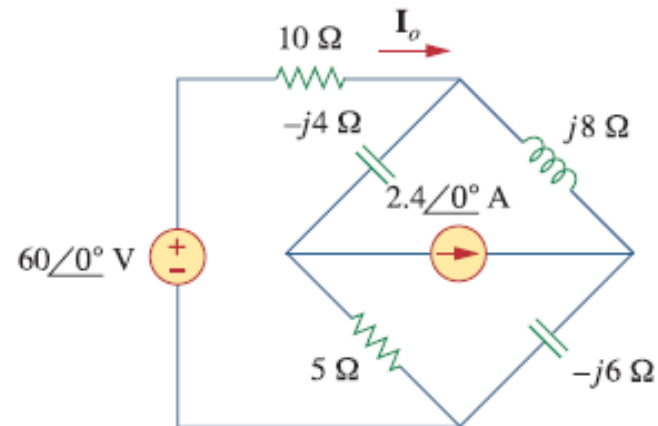


**Figure 10.11**

For Practice Prob. 10.4.

## Practice Problem 10.6

Calculate  $v_o$  in the circuit of Fig. 10.15 using the superposition theorem.

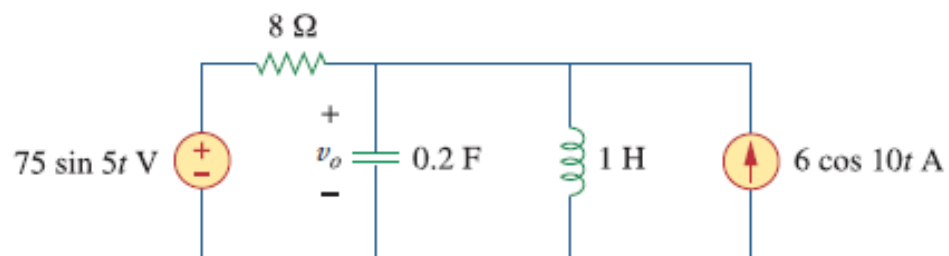


**Figure 10.15**

For Practice Prob. 10.6.

**Answer:**  $11.577 \sin(5t - 81.12^\circ) + 3.154 \cos(10t - 86.24^\circ) \text{ V}$ .

### Practice Problem 10.12

Obtain the closed-loop gain and phase shift for the circuit in Fig. 10.34. Let  $R = 10\text{ k}\Omega$ ,  $C = 1\text{ }\mu\text{F}$ , and  $\omega = 1000\text{ rad/s}$ .

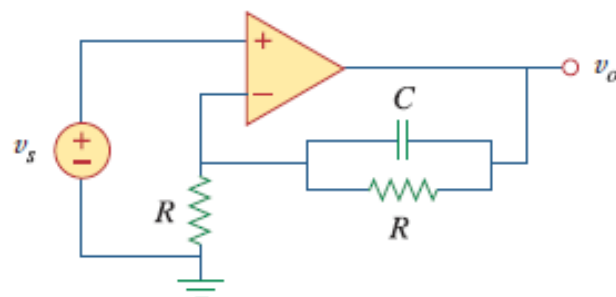

**Figure 10.34**


For Practice Prob. 10.12.

**Answer:** 1.0147,  $-5.6^\circ$ .

Determine the equivalent capacitance of the op amp circuit in Fig. 10.41 if  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 10 \text{ M}\Omega$ , and  $C = 10 \text{ nF}$ .

### Practice Problem 10.15

**Answer:**  $10 \mu\text{F}$ .

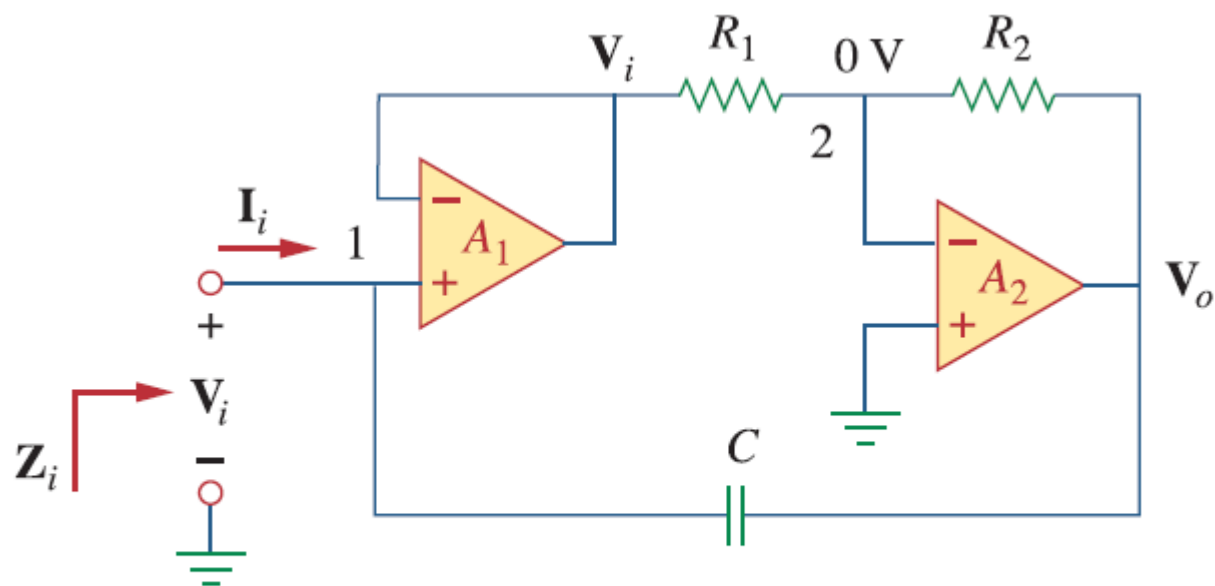


**Figure 10.41**  
Capacitance multiplier.

In the Wien-bridge oscillator circuit in Fig. 10.42, let  $R_1 = R_2 = 2.5 \text{ k}\Omega$ ,  $C_1 = C_2 = 1 \text{ nF}$ . Determine the frequency  $f_o$  of the oscillator.

### Practice Problem 10.16

**Answer:** 63.66 kHz.

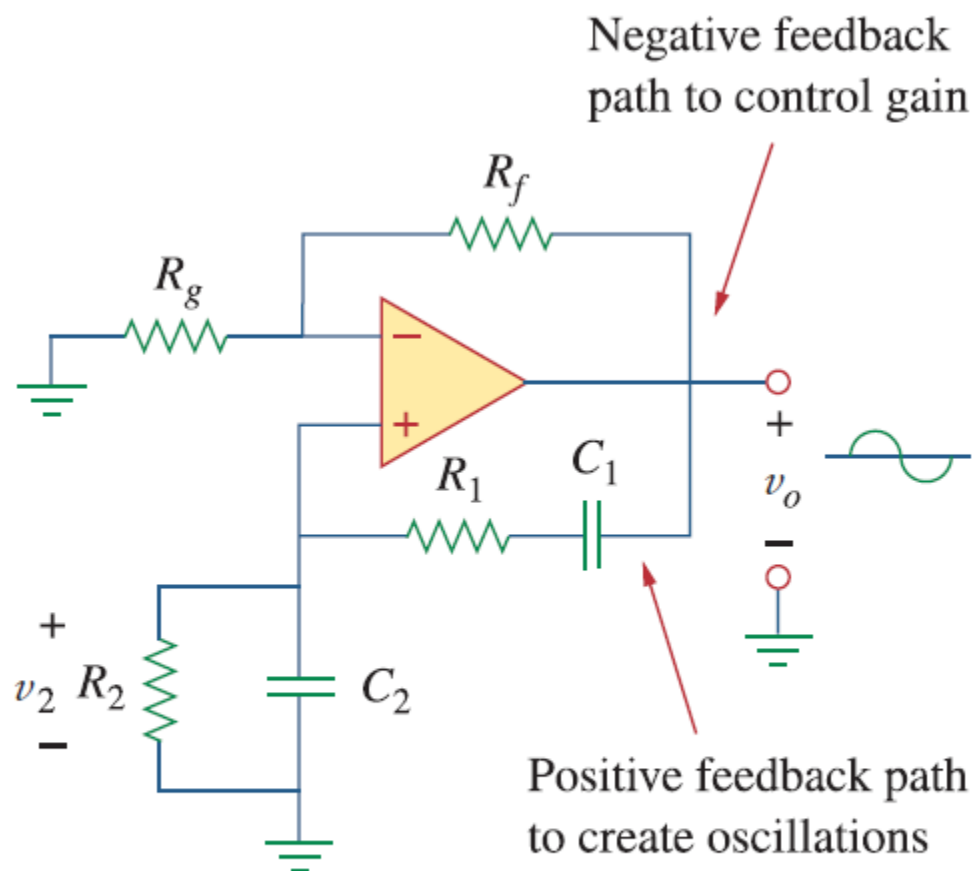

**Figure 10.42**

Wien-bridge oscillator.

- 10.2 (s10.2)
- 10.4 (s10.3)
- 10.6 (s10.4)
- 10.12 (s10.7)
- 10.15 (s10.9)
- 10.16 (s10.9)