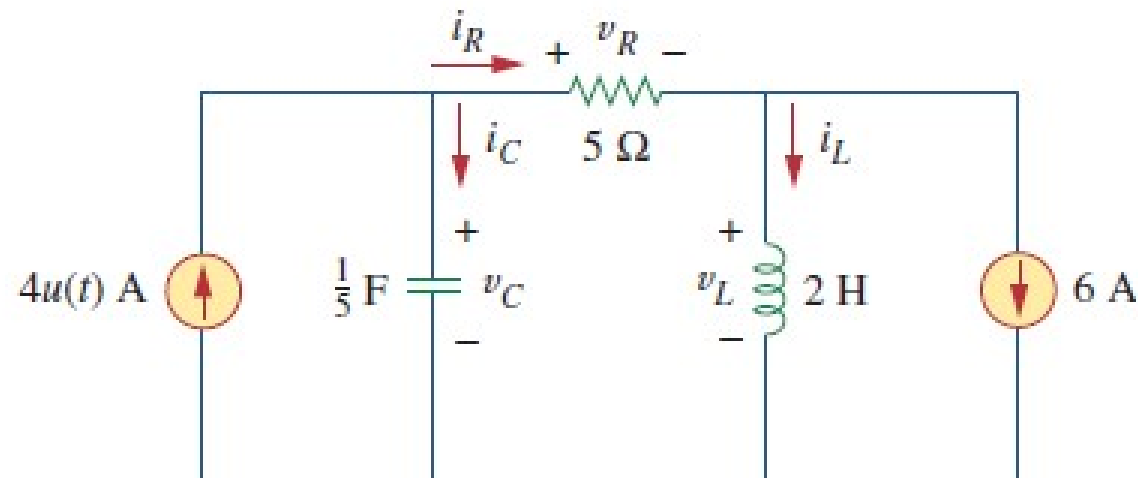


C8 problems

For the circuit in Fig. 8.7, find: (a) $i_L(0^+)$, $v_C(0^+)$, $v_R(0^+)$, (b) $di_L(0^+)/dt$, $dv_C(0^+)/dt$, $dv_R(0^+)/dt$, (c) $i_L(\infty)$, $v_C(\infty)$, $v_R(\infty)$.



Practice Problem 8.3


If $R = 10\ \Omega$, $L = 5\ \text{H}$, and $C = 2\ \text{mF}$,
What type of natural response will the circuit exhibit?

Refer to the circuit in Fig. 8.17. Find $v(t)$ for $t > 0$.

Answer: $150(e^{-10t} - e^{-2.5t})$ V.

Practice Problem 8.7

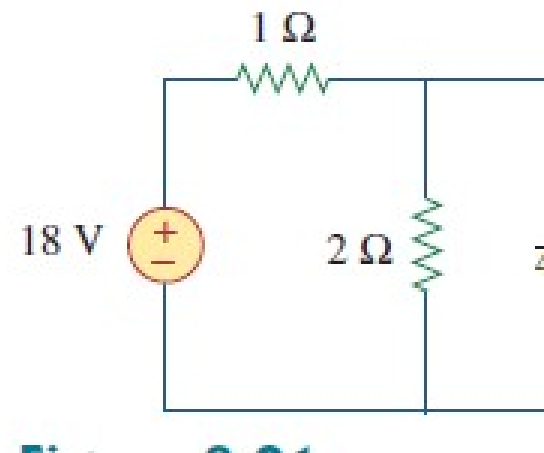Having been in position a for a long time, the switch is moved to position b at $t = 0$. Find the current i through the $2\ \Omega$ resistor for $t > 0$.




Determine v and i for $t > 0$ in the circuit of Fig. 8.28. (See comments about current sources in Practice Prob. 7.5.)

Answer: $12(1 - e^{-5t})$ V, $3(1 - e^{-5t})$ A.

Practice Problem 8.11

In the op amp circuit shown in Fig. 8.11, find $v_o(t)$ for $t > 0$. Assume that $R_1 = R_2 = 10\text{ k}\Omega$ and $C_1 = 10\text{ }\mu\text{F}$.

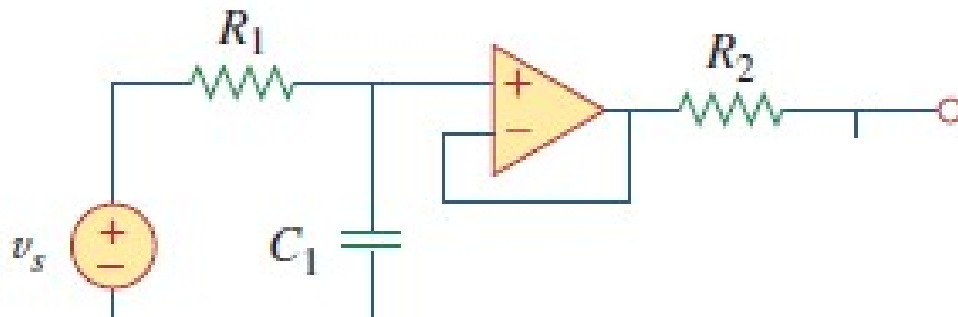
Answer: $(10 - 12.5e^{-t} + 2.5e^{-5})\text{ V}$



Practice Problem 8.15

For the circuit in Fig. 8.50, obtain


Answer: See Fig. 8.51.

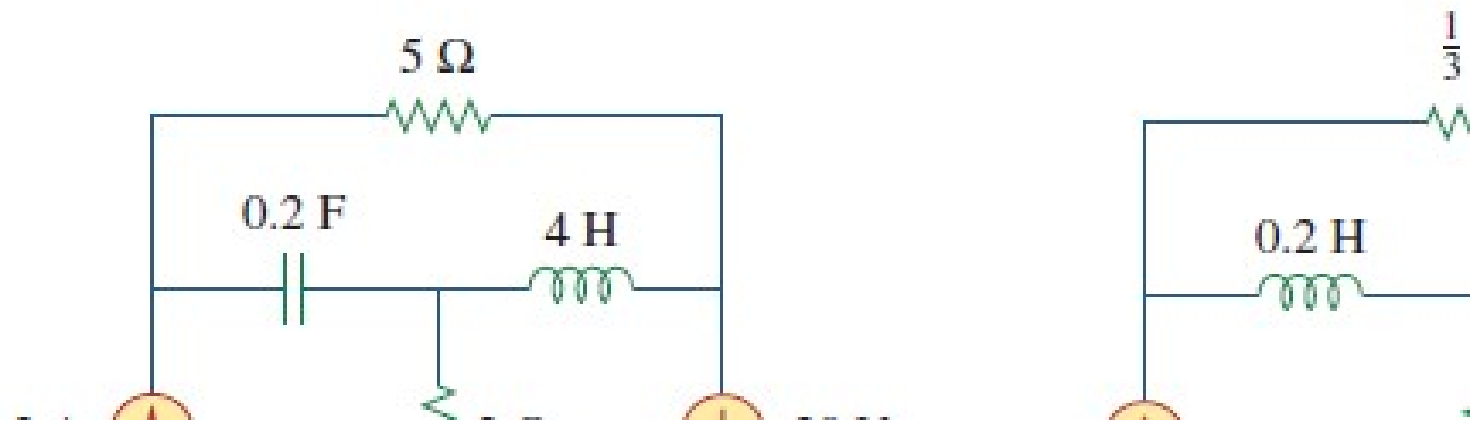

Practice Problem 8.15

For the circuit in Fig. 8.50, obtain

Answer: See Fig. 8.51.

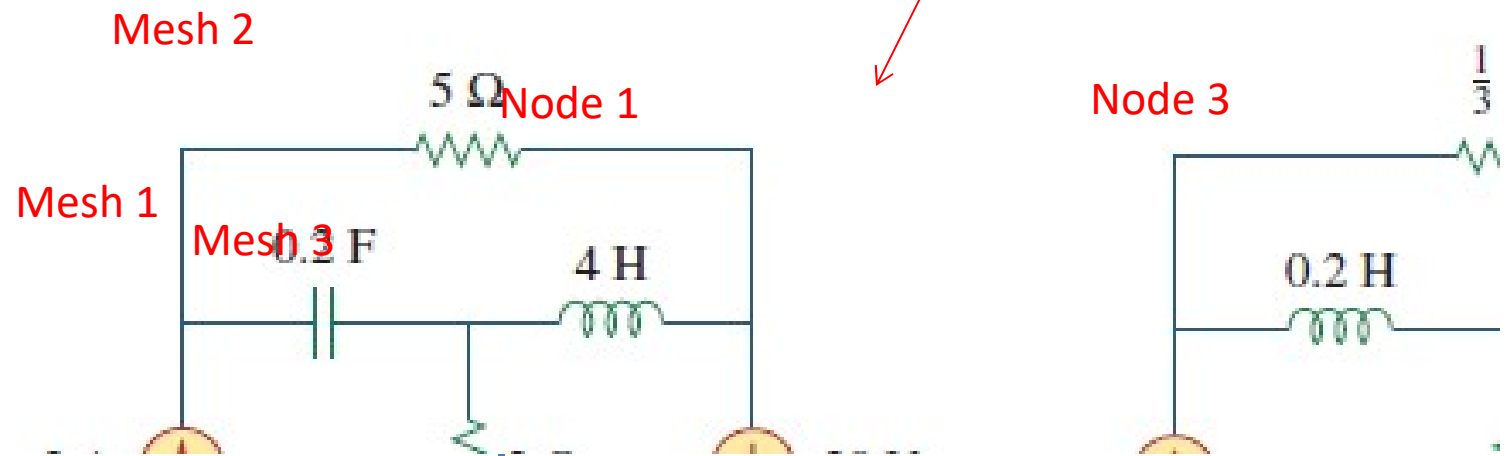

Mesh eq. for mesh 2:

$$5i_2 + 4\frac{d(i_2 - i_3)}{dt} + \frac{1}{0.2}\int(i_2 - i_1)dt = 0$$

Clockwise direction


Node eq. for node 2:

$$5v_2 + 4\frac{d(v_2 - v_3)}{dt} + \frac{1}{0.2}\int(v_2 - v_1)dt = 0$$

Leaving currents

Comparison of mesh eq. and nodal eq. in original and dual circuits:
By replacing i with v , we get totally same equations.

8.76 Find the dual of the circuit

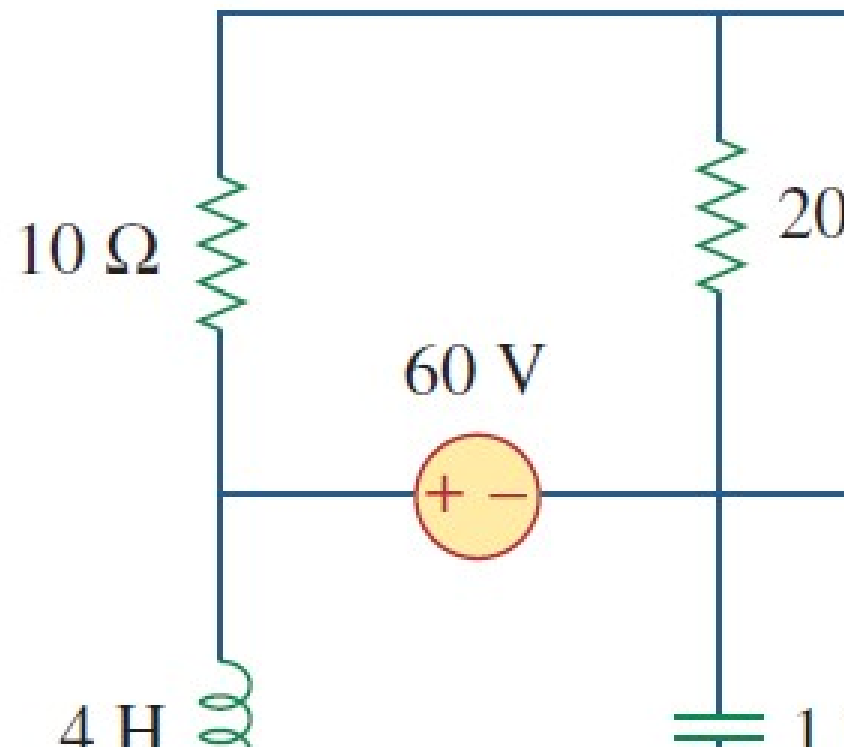

Mesh eq. 1: ... -60V ... = 0

Node eq. 1: ... -60A ... = 0

Leaving node 1 with -60A
→ Entering node 1 with 60A

- 8.2 (s8.2)
- 8.3 (s8.3)
- 8.6 (s8.4)
- 8.7 (s8.5)
- 8.9 (s8.7)
- 8.11 (s8.8)
- 8.15 (s8.10)