

Ve 216: Introduction to Signals and Systems

Yong Long

The University of Michigan- Shanghai Jiao Tong University Joint Institute
Shanghai Jiao Tong University

April 3, 2018

Based on Lecture Notes by Prof. Jeffrey A. Fessler

Outline

- 1 6. Applications of the FT: Filtering
 - Introduction
 - Ideal filters (6.3)
 - Real filters (6.4)
 - Bode Plots (6.2.3)
 - Bandwidth relationships
 - Summary

Outline

1 6. Applications of the FT: Filtering

- Introduction
- Ideal filters (6.3)
- Real filters (6.4)
- Bode Plots (6.2.3)
- Bandwidth relationships
- Summary

Applications of the FT

- In chapter 4 we covered all of the **fundamental mathematical properties** of the FT which are used in EE.
- These properties are not just “interesting math;” they are the **theoretical foundation** of how just about everything involving signals work, from AM radios to digital TVs to PC sound cards etc.
- Now (at last!) we can begin to use the **FT tools** to understand the basic principles behind some of these **applications**.

Applications of the FT

- In chapter 4 we covered all of the **fundamental mathematical properties** of the FT which are used in EE.
- These properties are not just “interesting math;” they are the **theoretical foundation** of how just about everything involving signals work, from AM radios to digital TVs to PC sound cards etc.
- Now (at last!) we can begin to use the **FT tools** to understand the basic principles behind some of these **applications**.

Applications of the FT

- In chapter 4 we covered all of the **fundamental mathematical properties** of the FT which are used in EE.
- These properties are not just “interesting math;” they are the **theoretical foundation** of how just about everything involving signals work, from AM radios to digital TVs to PC sound cards etc.
- Now (at last!) we can begin to use the **FT tools** to understand the basic principles behind some of these **applications**.

Overview

- **Filtering** (used universally)
convolution property
- **Modulation** (AM radio, digital comm (modems))
modulation property
- **Sampling** (A/D converters in sound cards)
FT of sampled signals
- ...

Overview

- **Filtering** (used universally)
convolution property
- **Modulation** (AM radio, digital comm (modems))
modulation property
- **Sampling** (A/D converters in sound cards)
FT of sampled signals
- ...

Overview

- **Filtering** (used universally)
convolution property
- **Modulation** (AM radio, digital comm (modems))
modulation property
- **Sampling** (A/D converters in sound cards)
FT of sampled signals
- ...

Outline

1 6. Applications of the FT: Filtering

- Introduction
- **Ideal filters (6.3)**
- Real filters (6.4)
- Bode Plots (6.2.3)
- Bandwidth relationships
- Summary

Output signal spectrum

The convolution property says that if

$$x(t) \rightarrow \boxed{\text{LTI } h(t)} \rightarrow y(t) = h(t) * x(t),$$

then

$$Y(\omega) = H(\omega)X(\omega).$$

- So the output signal spectrum is the input signal spectrum multiplied by $H(\omega)$.
- Some frequencies are attenuated, some are amplified, and others are possibly unchanged.

Output signal spectrum

The convolution property says that if

$$x(t) \rightarrow \boxed{\text{LTI } h(t)} \rightarrow y(t) = h(t) * x(t),$$

then

$$Y(\omega) = H(\omega)X(\omega).$$

- So the **output signal spectrum** is the **input signal spectrum** multiplied by $H(\omega)$.
- Some frequencies are **attenuated**, some are **amplified**, and others are possibly **unchanged**.

Output signal spectrum

The convolution property says that if

$$x(t) \rightarrow \boxed{\text{LTI } h(t)} \rightarrow y(t) = h(t) * x(t),$$

then

$$Y(\omega) = H(\omega)X(\omega).$$

- So the **output signal spectrum** is the **input signal spectrum** multiplied by $H(\omega)$.
- Some frequencies are **attenuated**, some are **amplified**, and others are possibly **unchanged**.

Output signal spectrum

In signal processing, often we are interested in selecting only a certain portion of the spectrum, and eliminating other portions.

Example

AM radio receiver must pass the signals in the frequency band transmitted by the radio station of interest, but remove all the other junk in the spectrum (such as other stations, TV signals, etc.).

Output signal spectrum

In signal processing, often we are interested in selecting only a certain portion of the spectrum, and eliminating other portions.

Example

AM radio receiver must pass the signals in the frequency band transmitted by the radio station of interest, but remove all the other junk in the spectrum (such as other stations, TV signals, etc.).

Ideal filters

Definition

Filters that pass unchanged a certain band of frequencies (called the **passband**) while completely removing other frequency components (called the **stopband**) are called **ideal filters**.

(*Picture*) of $|H(\omega)|$ with passband and stopband for

- 1 **lowpass** filter
- 2 **highpass** filter
- 3 **bandpass** filter
- 4 **bandstop** filter

Ideal filters

Definition


Filters that pass unchanged a certain band of frequencies (called the **passband**) while completely removing other frequency components (called the **stopband**) are called **ideal filters**.

(**Picture**) of $|H(\omega)|$ with passband and stopband for


- 1 **lowpass** filter
- 2 **highpass** filter
- 3 **bandpass** filter
- 4 **bandstop** filter

Lowpass and highpass filter

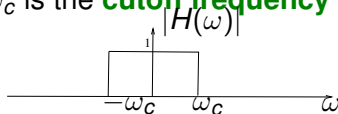
- 1 **lowpass** filter. ω_c is the **cutoff frequency**




- 2 **highpass** filter

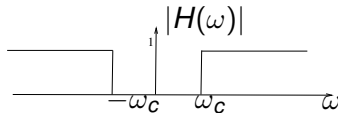

- 3 **bandpass** filter

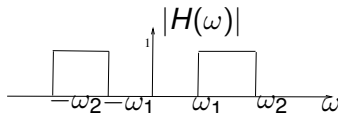

- 4 **bandstop** filter

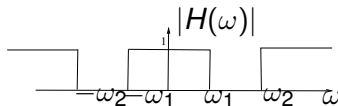

Ideal filters

These are called **ideal** filters because unfortunately we cannot build **real devices** with exactly those magnitude responses. We can come sufficiently close in practice, but not exactly.

- We will focus on **causal filters**, since those can be implemented in real time.
- Recall an LTI system is causal iff its **impulse response**

$$h(t) = 0 \text{ for } t < 0.$$

- If $h(t)$ is causal, then $H(\omega)$ cannot have any finite intervals where $H(\omega) = 0$, except if $h(t) = 0$.

Ideal filters

These are called **ideal** filters because unfortunately we cannot build **real devices** with exactly those magnitude responses. We can come sufficiently close in practice, but not exactly.

- We will focus on **causal filters**, since those can be implemented in real time.
- Recall an LTI system is causal iff its **impulse response**

$$h(t) = 0 \text{ for } t < 0.$$

- If $h(t)$ is causal, then $H(\omega)$ cannot have any finite intervals where $H(\omega) = 0$, except if $h(t) = 0$.

Ideal filters

These are called **ideal** filters because unfortunately we cannot build **real devices** with exactly those magnitude responses. We can come sufficiently close in practice, but not exactly.

-
- We will focus on **causal filters**, since those can be implemented in real time.
 - Recall an LTI system is causal iff its **impulse response**

$$h(t) = 0 \text{ for } t < 0.$$

- If $h(t)$ is causal, then $H(\omega)$ cannot have any finite intervals where $H(\omega) = 0$, except if $h(t) = 0$.

Ideal filters

These are called **ideal** filters because unfortunately we cannot build **real devices** with exactly those magnitude responses. We can come sufficiently close in practice, but not exactly.

-
- We will focus on **causal filters**, since those can be implemented in real time.
 - Recall an LTI system is causal iff its **impulse response**

$$h(t) = 0 \text{ for } t < 0.$$

- If $h(t)$ is causal, then $H(\omega)$ cannot have any finite intervals where $H(\omega) = 0$, except if $h(t) = 0$.

Ideal filters: example

Example

To see why, consider the **ideal lowpass filter**:

$$H(\omega) = \text{rect}\left(\frac{\omega}{2\omega_c}\right).$$

What is the impulse response $h(t)$? Taking the inverse FT using the FT table shows

$$h(t) = \frac{\omega_c}{\pi} \text{sinc}\left(\frac{\omega_c}{\pi} t\right) \xleftrightarrow{\mathcal{F}} H(\omega) = \text{rect}\left(\frac{\omega}{2\omega_c}\right).$$

(Picture)(MIT, Lecture 12, p.4)

Ideal filters: example

Example

To see why, consider the **ideal lowpass filter**:

$$H(\omega) = \text{rect}\left(\frac{\omega}{2\omega_c}\right).$$

What is the impulse response $h(t)$? Taking the inverse FT using the FT table shows

$$h(t) = \frac{\omega_c}{\pi} \text{sinc}\left(\frac{\omega_c}{\pi} t\right) \xleftrightarrow{\mathcal{F}} H(\omega) = \text{rect}\left(\frac{\omega}{2\omega_c}\right).$$

(Picture)(MIT, Lecture 12, p.4)

Ideal filters: example

- It is seen that the impulse response for this idea filter begins long before the impulse occurs at $t = 0$ (theoretically, at $t = -\infty$).
- Systems such as this, which respond to an input before the input is applied, are cllled **noncausal** systems.
- The physical existence of noncausal systems is impossible.
- Similar anayses could be used to show that ideal bandpass, ideal high-pass, and ideal bandstop filters are also physically unrealizable.
- However, the concept of noncausal systems, such as **idea filters**, can be **useful during the inital stages of a design or analysis effor**.

Ideal filters: example

- It is seen that the impulse response for this ideal filter begins long before the impulse occurs at $t = 0$ (theoretically, at $t = -\infty$).
- Systems such as this, which respond to an input before the input is applied, are called **noncausal** systems.
- **The physical existence of noncausal systems is impossible.**
- Similar analyses could be used to show that ideal bandpass, ideal high-pass, and ideal bandstop filters are also physically unrealizable.
- However, the concept of noncausal systems, such as **ideal filters**, can be **useful during the initial stages of a design or analysis effort**.

non-ideal filters

Question

Why non-ideal (real) filters?

non-ideal filters

Question

Why non-ideal (real) filters?

- *The above $h(t)$ is **noncausal!**, so no real system can implement it.*
- ***The ease of implementation.** In general, the more precisely we try to approximate or implement an ideal filter, the more complicated or costly the implementation becomes, whether in terms of components such as resistors, capacitors, and operational amplifiers.*
- ***Many applications do not need very sharp cutoff frequencies.** Video(MIT, Lecture 9, 31:40)*

Outline

1 6. Applications of the FT: Filtering

- Introduction
- Ideal filters (6.3)
- **Real filters (6.4)**
- Bode Plots (6.2.3)
- Bandwidth relationships
- Summary

Real filters

(Picture)(MIT, Lecture 12-5)

- A gradual **transition** region from passband with a cutoff frequency ω_p to stopband with a cutoff frequency of ω_s .
- A **deviation** from unity of $[1 - \delta_1, 1 + \delta_1]$ where $0 < \delta_1 \ll 1$ is allowed in the **passband**.
- A **deviation** of $0 < \delta_2 \ll 1$ from zero is allowed in the **stopband**.

Real filters

(Picture)(MIT, Lecture 12-5)

- A gradual **transition** region from passband with a cutoff frequency ω_p to stopband with a cutoff frequency of ω_s .
- A **deviation** from unity of $[1 - \delta_1, 1 + \delta_1]$ where $0 < \delta_1 \ll 1$ is allowed in the **passband**.
- A **deviation** of $0 < \delta_2 \ll 1$ from zero is allowed in the **stopband**.

Real filters


(Picture)(MIT, Lecture 12-5)

- A gradual **transition** region from passband with a cutoff frequency ω_p to stopband with a cutoff frequency of ω_s .
- A **deviation** from unity of $[1 - \delta_1, 1 + \delta_1]$ where $0 < \delta_1 \ll 1$ is allowed in the **passband**.
- A **deviation** of $0 < \delta_2 \ll 1$ from zero is allowed in the **stopband**.

Lowpass filter example (1)

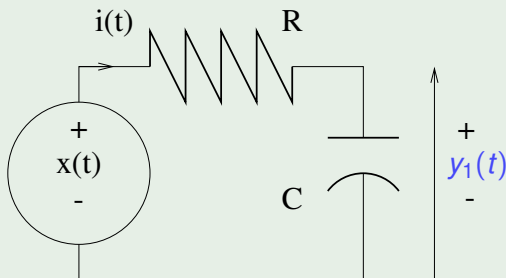
Example

Consider the following basic RC circuit, where the input signal $x(t)$ is the voltage source, and the output signal $y_1(t)$ is the voltage across the capacitor. Find the frequency response.




Lowpass filter example (1)
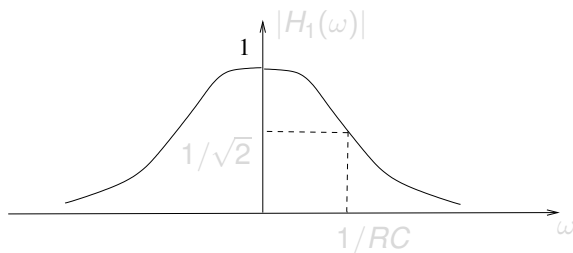
$$H_1(\omega) = \frac{Y_1(\omega)}{X(\omega)} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + RCj\omega}$$



Lowpass filter example (1)

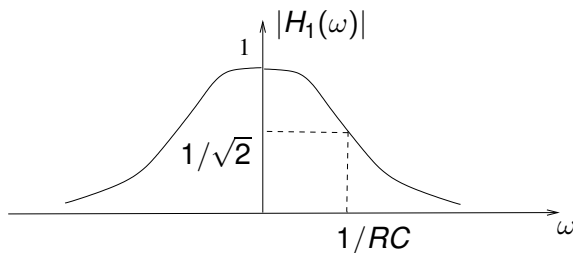
$$H_1(\omega) = \frac{Y_1(\omega)}{X(\omega)} = \frac{\frac{1}{j\omega C}}{\frac{1}{j\omega C} + R} = \frac{1}{1 + RCj\omega}$$



Highpass filter example (1)

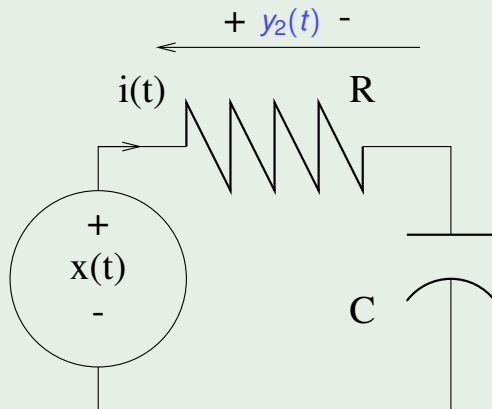
Example

Consider the following basic RC circuit, where the input signal $x(t)$ is the voltage source, and the output signal $y_2(t)$ is the voltage across the resistor. Find the frequency response.




Highpass filter example (2)
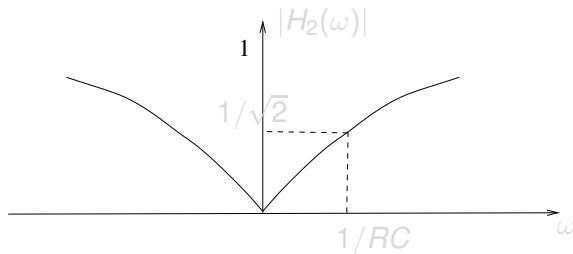
$$H_2(\omega) = \frac{Y_2(\omega)}{X(\omega)} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{RCj\omega}{1 + RCj\omega}$$




Highpass filter example (2)
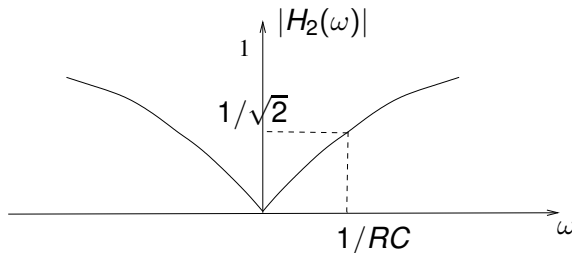
$$H_2(\omega) = \frac{Y_2(\omega)}{X(\omega)} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{RCj\omega}{1 + RCj\omega}$$



Real filters example

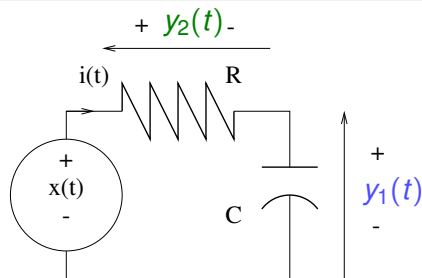


$$y_2(t) = x(t) - y_1(t) \implies Y_2(\omega) = X(\omega) - Y_1(\omega)$$

$$\implies \frac{Y_2(\omega)}{X(\omega)} = 1 - \frac{Y_1(\omega)}{X(\omega)} \implies H_2(\omega) = 1 - H_1(\omega)$$

Verify this relation:

$$\frac{1}{1 + RCj\omega} + \frac{RCj\omega}{1 + RCj\omega} = 1$$

Real filters example

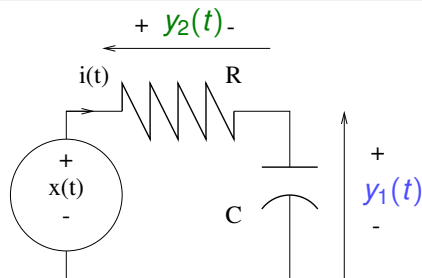


$$y_2(t) = x(t) - y_1(t) \implies Y_2(\omega) = X(\omega) - Y_1(\omega)$$

$$\implies \frac{Y_2(\omega)}{X(\omega)} = 1 - \frac{Y_1(\omega)}{X(\omega)} \implies H_2(\omega) = 1 - H_1(\omega)$$

Verify this relation:

$$\frac{1}{1 + RCj\omega} + \frac{RCj\omega}{1 + RCj\omega} = 1$$

Real filters example

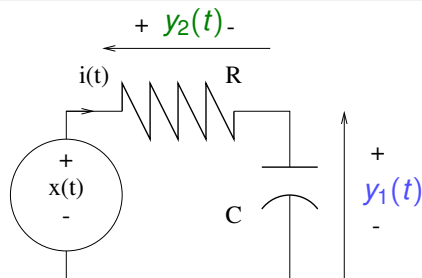

$$y_2(t) = x(t) - y_1(t) \implies Y_2(\omega) = X(\omega) - Y_1(\omega)$$

$$\implies \frac{Y_2(\omega)}{X(\omega)} = 1 - \frac{Y_1(\omega)}{X(\omega)} \implies H_2(\omega) = 1 - H_1(\omega)$$

Verify this relation:

$$\frac{1}{1 + RCj\omega} + \frac{RCj\omega}{1 + RCj\omega} = 1$$

Outline

1 6. Applications of the FT: Filtering

- Introduction
- Ideal filters (6.3)
- Real filters (6.4)
- **Bode Plots (6.2.3)**
- Bandwidth relationships
- Summary

Phase and magnitude relation

From the convolution property for CT FT, the FT of the output of an LTI system is related to the FT $X(\omega)$ to the system by the equation:

$$Y(\omega) = H(\omega)X(\omega) \implies |Y(\omega)|e^{j\angle Y(\omega)} = |H(\omega)|e^{j\angle H(\omega)}|X(\omega)|e^{j\angle X(\omega)}$$

Phase: addition

$$\angle Y(\omega) = \angle H(\omega) + \angle X(\omega)$$

Magnitude: multiplication

$$|Y(\omega)| = |H(\omega)||X(\omega)|$$

Magnitude on a logarithmic scale: addition

$$\log |Y(\omega)| = \log |H(\omega)| + \log |X(\omega)|$$

Phase and magnitude relation

From the convolution property for CT FT, the FT of the output of an LTI system is related to the FT $X(\omega)$ to the system by the equation:

$$Y(\omega) = H(\omega)X(\omega) \implies |Y(\omega)|e^{j\angle Y(\omega)} = |H(\omega)|e^{j\angle H(\omega)}|X(\omega)|e^{j\angle X(\omega)}$$

Phase: addition

$$\angle Y(\omega) = \angle H(\omega) + \angle X(\omega)$$

Magnitude: multiplication

$$|Y(\omega)| = |H(\omega)||X(\omega)|$$

Magnitude on a logarithmic scale: addition

$$\log |Y(\omega)| = \log |H(\omega)| + \log |X(\omega)|$$

Phase and magnitude relation

From the convolution property for CT FT, the FT of the output of an LTI system is related to the FT $X(\omega)$ to the system by the equation:

$$Y(\omega) = H(\omega)X(\omega) \implies |Y(\omega)|e^{j\angle Y(\omega)} = |H(\omega)|e^{j\angle H(\omega)}|X(\omega)|e^{j\angle X(\omega)}$$

Phase: addition

$$\angle Y(\omega) = \angle H(\omega) + \angle X(\omega)$$

Magnitude: multiplication

$$|Y(\omega)| = |H(\omega)||X(\omega)|$$

Magnitude on a logarithmic scale: addition

$$\log |Y(\omega)| = \log |H(\omega)| + \log |X(\omega)|$$

Phase and magnitude relation

From the convolution property for CT FT, the FT of the output of an LTI system is related to the FT $X(\omega)$ to the system by the equation:

$$Y(\omega) = H(\omega)X(\omega) \implies |Y(\omega)|e^{j\angle Y(\omega)} = |H(\omega)|e^{j\angle H(\omega)}|X(\omega)|e^{j\angle X(\omega)}$$

Phase: addition

$$\angle Y(\omega) = \angle H(\omega) + \angle X(\omega)$$

Magnitude: multiplication

$$|Y(\omega)| = |H(\omega)||X(\omega)|$$

Magnitude on a logarithmic scale: addition

$$\log |Y(\omega)| = \log |H(\omega)| + \log |X(\omega)|$$

Phase and magnitude plot

- If we have a graph of the log magnitude and phase of $X(\omega)$ and $H(\omega)$, the plot of $Y(\omega)$ is obtained by **adding the log-magnitude plots** and by **adding the phase plots**.
- The logarithmic scale allows detail to be displayed over a **wider** dynamic range.
- We can obtain plots of the log magnitude and phase of the overall frequency response of **cascaded systems** by **adding** the corresponding plots for each of the component systems.
e.g.,

$$H(\omega) = H_1(\omega)H_2(\omega)H_3(\omega).$$

Phase and magnitude plot

- If we have a graph of the log magnitude and phase of $X(\omega)$ and $H(\omega)$, the plot of $Y(\omega)$ is obtained by **adding the log-magnitude plots** and by **adding the phase plots**.
- The logarithmic scale allows detail to be displayed over a **wider** dynamic range.
- We can obtain plots of the log magnitude and phase of the overall frequency response of **cascaded systems** by **adding** the corresponding plots for each of the component systems.
e.g.,

$$H(\omega) = H_1(\omega)H_2(\omega)H_3(\omega).$$

Phase and magnitude plot

- If we have a graph of the log magnitude and phase of $X(\omega)$ and $H(\omega)$, the plot of $Y(\omega)$ is obtained by **adding the log-magnitude plots** and by **adding the phase plots**.
- The logarithmic scale allows detail to be displayed over a **wider** dynamic range.
- We can obtain plots of the log magnitude and phase of the overall frequency response of **cascaded systems** by **adding** the corresponding plots for each of the component systems.
e.g.,

$$H(\omega) = H_1(\omega)H_2(\omega)H_3(\omega).$$

Decibels

Definition

The specific logarithmic amplitude scale used is in units of $20 \log_{10}(\cdot)$, referred to as **decibels** (abbreviated **dB**).

magnitude	1	10	0.1	2
dB	0	20	-20	6

Definition

Plots of $20 \log_{10} |H(\omega)|$ and $\angle H(\omega)$ versus $\log_{10} \omega$ are referred to as **bode plots**.

(*Picture*)(MIT, Lecture 12-7)

Decibels

Definition

The specific logarithmic amplitude scale used is in units of $20 \log_{10}(\cdot)$, referred to as **decibels** (abbreviated **dB**).

magnitude	1	10	0.1	2
dB	0	20	-20	6

Definition

Plots of $20 \log_{10} |H(\omega)|$ and $\angle H(\omega)$ versus $\log_{10} \omega$ are referred to as **bode plots**.

(*Picture*)(MIT, Lecture 12-7)

Decibels

Definition

The specific logarithmic amplitude scale used is in units of $20 \log_{10}(\cdot)$, referred to as **decibels** (abbreviated **dB**).

magnitude	1	10	0.1	2
dB	0	20	-20	6

Definition

Plots of $20 \log_{10} |H(\omega)|$ and $\angle H(\omega)$ versus $\log_{10} \omega$ are referred to as **bode plots**.

(Picture)(MIT, Lecture 12-7)

Bode plots

- Recall if $h(t)$ is **real**

$$H(\omega) = H^*(-\omega)$$

$$|H(\omega)| = |H(-\omega)|, \quad \angle H(\omega) = -\angle H(-\omega)$$

- The plots for $\omega < 0$ are **superfluous** and can be obtained immediately from the plots for $\omega \geq 0$.
- This makes it possible to plot logarithmic frequency versus $\log_{10} \omega$ for $\omega \geq 0$.

Recording control room example

Bode plots

- Recall if $h(t)$ is **real**

$$H(\omega) = H^*(-\omega)$$

$$|H(\omega)| = |H(-\omega)|, \quad \angle H(\omega) = -\angle H(-\omega)$$

- The plots for $\omega < 0$ are **superfluous** and can be obtained immediately from the plots for $\omega \geq 0$.
- This makes it possible to plot logarithmic frequency versus $\log_{10} \omega$ for $\omega \geq 0$.

Recording control room example

Bode plots

- Recall if $h(t)$ is **real**

$$H(\omega) = H^*(-\omega)$$

$$|H(\omega)| = |H(-\omega)|, \quad \angle H(\omega) = -\angle H(-\omega)$$

- The plots for $\omega < 0$ are **superfluous** and can be obtained immediately from the plots for $\omega \geq 0$.
- This makes it possible to plot logarithmic frequency versus $\log_{10} \omega$ for $\omega \geq 0$.

Recording control room example

Bode plots

- Recall if $h(t)$ is **real**

$$H(\omega) = H^*(-\omega)$$

$$|H(\omega)| = |H(-\omega)|, \quad \angle H(\omega) = -\angle H(-\omega)$$

- The plots for $\omega < 0$ are **superfluous** and can be obtained immediately from the plots for $\omega \geq 0$.
- This makes it possible to plot logarithmic frequency versus $\log_{10} \omega$ for $\omega \geq 0$.

Recording control room example

Bode plots

- Recall if $h(t)$ is **real**

$$H(\omega) = H^*(-\omega)$$

$$|H(\omega)| = |H(-\omega)|, \quad \angle H(\omega) = -\angle H(-\omega)$$

- The plots for $\omega < 0$ are **superfluous** and can be obtained immediately from the plots for $\omega \geq 0$.
- This makes it possible to plot logarithmic frequency versus $\log_{10} \omega$ for $\omega \geq 0$.

Recording control room example

Graphic equalizer

Definition

A **graphic equalizer** is a high-fidelity audio control that allows the user to see graphically and control individually a number of different frequency bands in a stereophonic system.

Definition

In sound recording and reproduction, **equalization** is the process commonly used to alter the frequency response of an audio system using linear filters.

[Video](#) (MIT, Lecture 12, 19:40-27:25min)

Graphic equalizer

Definition

A **graphic equalizer** is a high-fidelity audio control that allows the user to see graphically and control individually a number of different frequency bands in a stereophonic system.

Definition

In sound recording and reproduction, **equalization** is the process commonly used to alter the frequency response of an audio system using linear filters.

[Video](#) (MIT, Lecture 12, 19:40-27:25min)

Graphic equalizer

Definition

A **graphic equalizer** is a high-fidelity audio control that allows the user to see graphically and control individually a number of different frequency bands in a stereophonic system.

Definition

In sound recording and reproduction, **equalization** is the process commonly used to alter the frequency response of an audio system using linear filters.

[Video](#) (MIT, Lecture 12, 19:40-27:25min)

Outline

1 6. Applications of the FT: Filtering

- Introduction
- Ideal filters (6.3)
- Real filters (6.4)
- Bode Plots (6.2.3)
- **Bandwidth relationships**
- Summary

RMS bandwidth

Definition

For symmetric spectra, **root mean-squared bandwidth** or **RMS bandwidth** is defined as

$$\omega_{\text{rms}} \triangleq \sqrt{\frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega}}$$

Example

Find the RMS bandwidth of the Gaussian signal

$$x(t) = e^{-(t/t_0)^2}, \quad \text{for } t_0 > 0$$

RMS bandwidth

Definition

For symmetric spectra, **root mean-squared bandwidth** or **RMS bandwidth** is defined as

$$\omega_{\text{rms}} \triangleq \sqrt{\frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega}}$$

Example

Find the RMS bandwidth of the Gaussian signal

$$x(t) = e^{-(t/t_0)^2}, \quad \text{for } t_0 > 0$$

RMS bandwidth: solution

By the FT table

$$x(t) = e^{-(t/t_0)^2} \xleftrightarrow{\mathcal{F}} X(\omega) = t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2}$$

$$\begin{aligned} \omega_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega} = \frac{\int_{-\infty}^{\infty} \omega^2 (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega}{\int_{-\infty}^{\infty} (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega} \\ &= \frac{t_0^{-1} \int_{-\infty}^{\infty} x^2 (\sqrt{\pi} e^{-(x/2)^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (\sqrt{\pi} e^{-(x/2)^2})^2 dx} \quad (x = \omega t_0, d\omega = dx/t_0) \\ &= \frac{1}{t_0^2} \frac{\pi^{3/2} \sqrt{2}}{\pi^{3/2} \sqrt{2}} = \frac{1}{t_0^2} \end{aligned}$$

Thus

$$\boxed{\omega_{\text{rms}} = \frac{1}{t_0}}$$

RMS bandwidth: solution

By the FT table

$$x(t) = e^{-(t/t_0)^2} \xleftrightarrow{\mathcal{F}} X(\omega) = t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2}$$

$$\begin{aligned} \omega_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega} = \frac{\int_{-\infty}^{\infty} \omega^2 (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega}{\int_{-\infty}^{\infty} (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega} \\ &= \frac{t_0^{-1} \int_{-\infty}^{\infty} x^2 (\sqrt{\pi} e^{-(x/2)^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (\sqrt{\pi} e^{-(x/2)^2})^2 dx} \quad (x = \omega t_0, d\omega = dx/t_0) \\ &= \frac{1}{t_0^2} \frac{\pi^{3/2} \sqrt{2}}{\pi^{3/2} \sqrt{2}} = \frac{1}{t_0^2} \end{aligned}$$

Thus

$$\boxed{\omega_{\text{rms}} = \frac{1}{t_0}}$$

RMS bandwidth: solution

By the FT table

$$x(t) = e^{-(t/t_0)^2} \xleftrightarrow{\mathcal{F}} X(\omega) = t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2}$$

$$\begin{aligned} \omega_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega} = \frac{\int_{-\infty}^{\infty} \omega^2 (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega}{\int_{-\infty}^{\infty} (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega} \\ &= \frac{t_0^{-1} \int_{-\infty}^{\infty} x^2 (\sqrt{\pi} e^{-(x/2)^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (\sqrt{\pi} e^{-(x/2)^2})^2 dx} \quad (x = \omega t_0, d\omega = dx/t_0) \\ &= \frac{1}{t_0^2} \frac{\pi^{3/2} \sqrt{2}}{\pi^{3/2} \sqrt{2}} = \frac{1}{t_0^2} \end{aligned}$$

Thus

$$\boxed{\omega_{\text{rms}} = \frac{1}{t_0}}$$

RMS bandwidth: solution

By the FT table

$$x(t) = e^{-(t/t_0)^2} \xleftrightarrow{\mathcal{F}} X(\omega) = t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2}$$

$$\begin{aligned} \omega_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} \omega^2 |X(\omega)|^2 d\omega}{\int_{-\infty}^{\infty} |X(\omega)|^2 d\omega} = \frac{\int_{-\infty}^{\infty} \omega^2 (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega}{\int_{-\infty}^{\infty} (t_0 \sqrt{\pi} e^{-(\omega t_0/2)^2})^2 d\omega} \\ &= \frac{t_0^{-1} \int_{-\infty}^{\infty} x^2 (\sqrt{\pi} e^{-(x/2)^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (\sqrt{\pi} e^{-(x/2)^2})^2 dx} \quad (x = \omega t_0, d\omega = dx/t_0) \\ &= \frac{1}{t_0^2} \frac{\pi^{3/2} \sqrt{2}}{\pi^{3/2} \sqrt{2}} = \frac{1}{t_0^2} \end{aligned}$$


Thus

$$\boxed{\omega_{\text{rms}} = \frac{1}{t_0}}$$


Time duration definitions

- For **time-limited** signal, **absolute time duration**

$$\tau = t_2 - t_1.$$

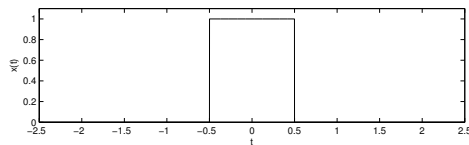

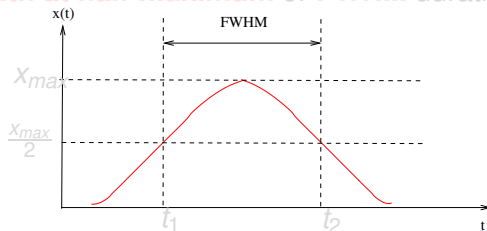
- For **non-time-limited** signals, an frequently-used measure is the **full-width at half-maximum** or **FWHM** duration.




Time duration definitions

- For **time-limited** signal, **absolute time duration**

$$\tau = t_2 - t_1.$$

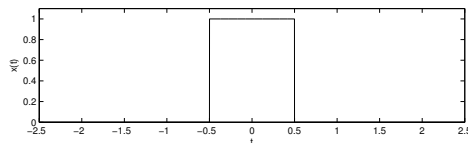

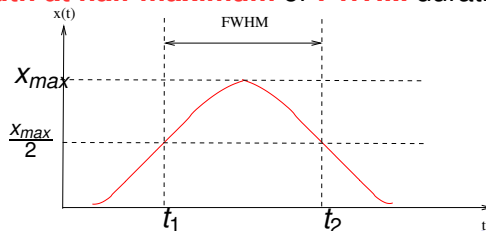- For **non-time-limited** signals, an frequently-used measure is the **full-width at half-maximum** or **FWHM** duration.



RMS time duration

Definition

For symmetric signals, **root mean-squared time duration** or **RMS time duration** is defined as

$$\tau_{\text{rms}} \triangleq \sqrt{\frac{\int_{-\infty}^{\infty} t^2 |x(t)|^2 dt}{\int_{-\infty}^{\infty} |x(t)|^2 dt}}$$

Example

Find the RMS time duration of the Gaussian signal

$$x(t) = e^{-(t/t_0)^2}, \quad \text{for } t_0 > 0$$

RMS time duration: solution

$$\begin{aligned}
 \tau_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} t^2 |x(t)|^2 dt}{\int_{-\infty}^{\infty} |x(t)|^2 dt} = \frac{\int_{-\infty}^{\infty} t^2 (e^{-(t/t_0)^2})^2 dt}{\int_{-\infty}^{\infty} (e^{-(t/t_0)^2})^2 dt} \\
 &= \frac{t_0^3 \int_{-\infty}^{\infty} x^2 (e^{-x^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (e^{-x^2})^2 dx} \quad (x = t/t_0, dt = t_0 dx) \\
 &= t_0^2 \frac{\sqrt{2\pi}/8}{\sqrt{\pi}/2} = \frac{t_0^2}{4}
 \end{aligned}$$

Thus

$$\tau_{\text{rms}} = \frac{t_0}{2}$$

RMS time duration: solution

$$\begin{aligned}
 \tau_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} t^2 |x(t)|^2 dt}{\int_{-\infty}^{\infty} |x(t)|^2 dt} = \frac{\int_{-\infty}^{\infty} t^2 (e^{-(t/t_0)^2})^2 dt}{\int_{-\infty}^{\infty} (e^{-(t/t_0)^2})^2 dt} \\
 &= \frac{t_0^3 \int_{-\infty}^{\infty} x^2 (e^{-x^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (e^{-x^2})^2 dx} \quad (x = t/t_0, dt = t_0 dx) \\
 &= t_0^2 \frac{\sqrt{2\pi}/8}{\sqrt{\pi}/2} = \frac{t_0^2}{4}
 \end{aligned}$$

Thus

$$\tau_{\text{rms}} = \frac{t_0}{2}$$

RMS time duration: solution

$$\begin{aligned}
 \tau_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} t^2 |x(t)|^2 dt}{\int_{-\infty}^{\infty} |x(t)|^2 dt} = \frac{\int_{-\infty}^{\infty} t^2 (e^{-(t/t_0)^2})^2 dt}{\int_{-\infty}^{\infty} (e^{-(t/t_0)^2})^2 dt} \\
 &= \frac{t_0^3 \int_{-\infty}^{\infty} x^2 (e^{-x^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (e^{-x^2})^2 dx} \quad (x = t/t_0, dt = t_0 dx) \\
 &= t_0^2 \frac{\sqrt{2\pi}/8}{\sqrt{\pi}/2} = \frac{t_0^2}{4}
 \end{aligned}$$

Thus

$$\tau_{\text{rms}} = \frac{t_0}{2}$$

RMS time duration: solution

$$\begin{aligned}
 \tau_{\text{rms}}^2 &= \frac{\int_{-\infty}^{\infty} t^2 |x(t)|^2 dt}{\int_{-\infty}^{\infty} |x(t)|^2 dt} = \frac{\int_{-\infty}^{\infty} t^2 (e^{-(t/t_0)^2})^2 dt}{\int_{-\infty}^{\infty} (e^{-(t/t_0)^2})^2 dt} \\
 &= \frac{t_0^3 \int_{-\infty}^{\infty} x^2 (e^{-x^2})^2 dx}{t_0 \int_{-\infty}^{\infty} (e^{-x^2})^2 dx} \quad (x = t/t_0, dt = t_0 dx) \\
 &= t_0^2 \frac{\sqrt{2\pi}/8}{\sqrt{\pi}/2} = \frac{t_0^2}{4}
 \end{aligned}$$

Thus

$$\boxed{\tau_{\text{rms}} = \frac{t_0}{2}}$$

Time-bandwidth product

Using the Cauchy-Schwarz inequality, one can show (for signals satisfying certain regularity conditions):

$$\omega_{\text{rms}} \tau_{\text{rms}} \geq \frac{1}{2}.$$

The time duration of a signal and its frequency bandwidth are inversely related. A signal cannot be localized in both time and in frequency..

Extreme cases:

- **impulse function**: narrow in time, wide spectrum
- **sinusoid signal**: periodic (infinite duration) in time, narrow spectrum
- **gaussian signal**: time-bandwidth product is as narrow as possible

Time-bandwidth product

Using the Cauchy-Schwarz inequality, one can show (for signals satisfying certain regularity conditions):

$$\omega_{\text{rms}} \tau_{\text{rms}} \geq \frac{1}{2}.$$

The time duration of a signal and its frequency bandwidth are inversely related. A signal cannot be localized in both time and in frequency..

Extreme cases:

- **impulse function**: narrow in time, wide spectrum
- **sinusoid signal**: periodic (infinite duration) in time, narrow spectrum
- **gaussian signal**: time-bandwidth product is as narrow as possible

Time-bandwidth product

Using the Cauchy-Schwarz inequality, one can show (for signals satisfying certain regularity conditions):

$$\omega_{\text{rms}} \tau_{\text{rms}} \geq \frac{1}{2}.$$

The time duration of a signal and its frequency bandwidth are inversely related. A signal cannot be localized in both time and in frequency..

Extreme cases:

- **impulse function**: narrow in time, wide spectrum
- **sinusoid signal**: periodic (infinite duration) in time, narrow spectrum
- **gaussian signal**: time-bandwidth product is as narrow as possible

Time-bandwidth product: example

Example

Compute the time-bandwidth product of

$$x(t) = \text{tri}(t)$$

Time-bandwidth product: solution (1)

$$x(t) = \text{tri}(t) \xleftrightarrow{\mathcal{F}} X(\omega) = \text{sinc}^2(\omega/2)$$

$$\omega_{\text{rms}} = \frac{\int_0^\infty \omega^2 [\text{sinc}^2(\omega/2)]^2 d\omega}{\int_0^\infty [\text{sinc}^2(\omega/2)]^2 d\omega} = \frac{2\pi}{2\pi/3} = 3$$

so

$$\omega_{\text{rms}} = \sqrt{3} \approx 1.73$$

Time-bandwidth product: solution (1)

$$x(t) = \text{tri}(t) \xleftrightarrow{\mathcal{F}} X(\omega) = \text{sinc}^2(\omega/2)$$

$$\omega_{\text{rms}} = \frac{\int_0^\infty \omega^2 [\text{sinc}^2(\omega/2)]^2 d\omega}{\int_0^\infty [\text{sinc}^2(\omega/2)]^2 d\omega} = \frac{2\pi}{2\pi/3} = 3$$

so

$$\omega_{\text{rms}} = \sqrt{3} \approx 1.73$$

Time-bandwidth product: solution (2)

$$\tau_{\text{rms}}^2 = \frac{\int_0^1 t^2(1-t)^2 dt}{\int_0^1 (1-t)^2 dt} = \frac{1/30}{1/3} = \frac{1}{10}$$

so

$$\tau_{\text{rms}} = 1/\sqrt{10} \approx 0.32$$

Thus

$$\omega_{\text{rms}} \tau_{\text{rms}} = \sqrt{3/10} \approx \boxed{0.548} \geq 1/2$$

but fairly close.

Time-bandwidth product: solution (2)

$$\tau_{\text{rms}}^2 = \frac{\int_0^1 t^2(1-t)^2 dt}{\int_0^1 (1-t)^2 dt} = \frac{1/30}{1/3} = \frac{1}{10}$$

so

$$\tau_{\text{rms}} = 1/\sqrt{10} \approx 0.32$$

Thus

$$\omega_{\text{rms}} \tau_{\text{rms}} = \sqrt{3/10} \approx \boxed{0.548} \geq 1/2$$

but fairly close.

Outline

- 1 6. Applications of the FT: Filtering
 - Introduction
 - Ideal filters (6.3)
 - Real filters (6.4)
 - Bode Plots (6.2.3)
 - Bandwidth relationships
 - **Summary**

Summary

- ideal filters
- real filters
- bode plots
- bandwidth
- time-bandwidth product